

**DIGITAL SYSTEM DESIGN**  
**(EE-326-F)**

**LAB MANUAL**

**VI SEMESTER**



**DRONACHARYA**  
College of Engineering

*Department Of Electronics & Communication Engg*  
*Dronacharya College Of Engineering*  
*Khentawas, Gurgaon – 123506*

**LIST OF EXPERIMENTS**



S.NO.	NAME OF THE EXPERIMENT	Page No.
<b>PERFORM ANY FIVE EXPERIMENT USING VHDL</b>		
1	Design all gates using VHDL.	3
2	Write VHDL programs for the following circuits, check the wave forms and the hardware generated a. Half adder            b. Full adder	7
3	Write VHDL programs for the following circuits, check the wave forms and the hardware generated a. Multiplexer            b. Demultiplexer	13
4	Write VHDL program for encoder and check the wave forms and the hardware generated.	19
5	Write a VHDL program for a decoder and check the wave forms and the hardware generated.	22
6	Write a VHDL program for a Down counter and check the wave forms and the hardware generated.	25
7	Write a VHDL program for a BCD to GRAY code converter and check the wave forms and the hardware generated.	28
8	Write a VHDL program for a T FLIP-FLOP and check the wave forms and the hardware generated.	31
<b>PERFORM ANY FIVE EXPERIMENT USING FPGA AND CPLD</b>		
9	Implement Half Adder using FPGA & CPLD.	34
10	Implement Full Adder using FPGA & CPLD.	35
11	Implement Delay Flip flop using FPGA & CPLD.	38
12	Implement BCD to 7 segments Decoder using FPGA& CPLD.	41
13	Implement an Up Counter using FPGA & CPLD.	44
14	Implement 1-bit Comparator using FPGA & CPLD .	47
15	Implement ALU using FPGA & CPLD.	49

## EXPERIMENT No. 1

**Aim:- To Design Logic Gates using VHDL**

  **LOGIC GATES:**


A logic gate performs a logical operation on one or more logic inputs and produces a single logic output. The logic normally performed is Boolean logic and is most commonly found in digital circuits. Logic gates are primarily implemented electronically using diodes or transistors, but can also be constructed using electromagnetic relays (relay logic), fluidic logic, pneumatic logic, optics, molecules, or even mechanical elements.



INPUT		OUTPUT
A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1




INPUT		OUTPUT
A	B	A OR B
0	0	0
0	1	1
1	0	1
1	1	1

 

INPUT	OUTPUT
A	NOT A
0	1
1	0

 
In electronics a NOT gate is more commonly called an inverter. The circle on the symbol is called a *bubble*, and is generally used in circuit diagrams to indicate an inverted (active-low) input or output.




INPUT		OUTPUT
A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0

# DIGITAL SYSTEM DESIGN (EE-326-F)


---

 

INPUT		OUTPUT
A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

 

INPUT		OUTPUT
A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

 

INPUT		OUTPUT
A	B	A XNOR B
0	0	1
0	1	0
1	0	0
1	1	1

---

## Program:

```
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity all_ga is  
  Port ( a : in STD_LOGIC;  
        b : in STD_LOGIC;  
        c : out STD_LOGIC;  
        c1 : out STD_LOGIC;  
        c2 : out STD_LOGIC;  
        c3 : out STD_LOGIC;  
        c4 : out STD_LOGIC;  
        c5 : out STD_LOGIC;  
        c6 : out STD_LOGIC);  
end all_ga;
```


```
architecture Behavioral of all_ga is
```

```
begin  
  c <= a and b;  
  c1 <= a or b;  
  c2 <= a nand b;  
  c3 <= a nor b;  
  c4 <= a xor b;  
  c5 <= a xnor b;  
  c6 <= not b;
```


```
end Behavioral;
```

## OUTPUT:

RTL View

 

Simulation Waveform

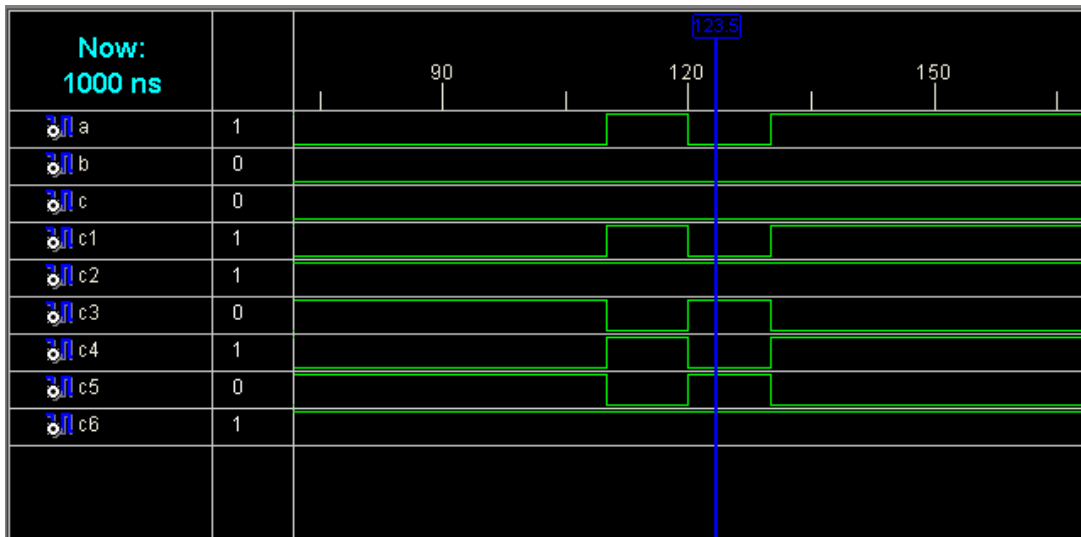

### Quiz Questions with answer.

Q.1 What is VHDL?

Ans. VHDL is the VHSIC Hardware Description Language. VHSIC is an abbreviation for Very High Speed Integrated Circuit.

Q.2 How many truth table entries are necessary for a four-input circuit?

Ans. 16

Q.3 What input values will cause an AND logic gate to produce a HIGH output?

Ans. All inputs of AND gate must be HIGH.

Q.4 Name all the basic gates.

Ans. i) AND ii) OR iii) NOT

Q.5 Name all the universal gates.

Ans. i) NAND ii) NOR

Q.6 What is the full form of IEEE?

Ans. Institute of Electrical and Electronic Engineering.

Q.7. What is the full form of ASCII?

Ans. American Standard Code for information Interchange.

Q.8. Define Entity.

Ans. It is an external view of a design unit.

Q.9. Why NAND and NOR are called universal gates?

Ans. Because all the basic gates can be derive from them.

Q.10. How many architectures are present in VHDL.

Ans. 4, behavior, dataflow, structural and mixed.

## EXPERIMENT No. 2 (A)

**Aim:- To Design a Half Adder using VHDL**

### Half adder


A **half adder** is a logical circuit that performs an addition operation on two one-bit binary numbers often written as  $A$  and  $B$ .

The half adder output is a sum of the two inputs usually represented with the signals  $C_{out}$  and  $S$  where

$$sum = 2 \times C_{out} + S.$$

Following is the logic table and circuit diagram for half adder:

Inputs		Outputs	
$A$	$B$	$C$	$S$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


## Program:

```
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
---- Uncomment the following library declaration if instantiating  
---- any Xilinx primitives in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
entity ha is  
    Port ( a : in STD_LOGIC;  
          b : in STD_LOGIC;  
          s : out STD_LOGIC;  
          c : out STD_LOGIC);  
end ha;  
  
architecture Behavioral of ha is  
begin  
s <= a xor b;  
c <= a and b;  
end Behavioral;
```


## OUTPUT:

RTL View

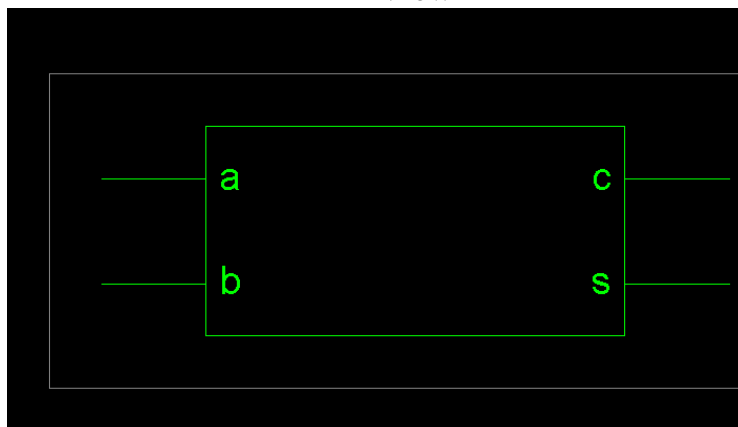



Simulation Waveform

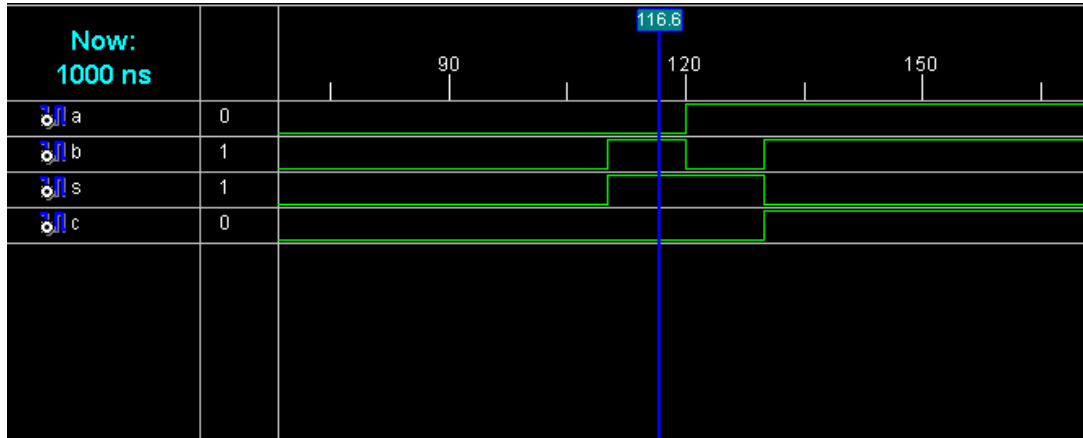

## EXPERIMENT No. 2 (B)

**Aim:- To Design a Full Adder using VHDL**

### Full adder


A **full adder** is a logical circuit that performs an addition operation on three one-bit binary numbers often written as  $A$ ,  $B$ , and  $C_{in}$ . The full adder produces a two-bit output sum typically represented with the signals  $C_{out}$  and  $S$  where

$$sum = 2 \times C_{out} + S.$$

The full adder's truth table is:

Truth Table:

Inputs			Outputs	
$A$	$B$	$C_i$	$C_o$	$S$
0	0	0	0	0
1	0	0	0	1
0	1	0	0	1
1	1	0	1	0
0	0	1	0	1
1	0	1	1	0
0	1	1	1	0
1	1	1	1	1

 


## Program:


```
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
---- Uncomment the following library declaration if instantiating  
---- any Xilinx primitives in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
entity fa is  
    Port ( a : in STD_LOGIC;  
          b : in STD_LOGIC;  
          cin : in STD_LOGIC;  
          s : out STD_LOGIC;  
          cout : out STD_LOGIC);  
end fa;  
  
architecture Behavioral of fa is  
  
begin  
s <= (a xor b) xor cin;  
cout <= (a and b) or (b and cin) or (a and cin);  
  
end Behavioral;
```

## OUTPUT:

RTL View

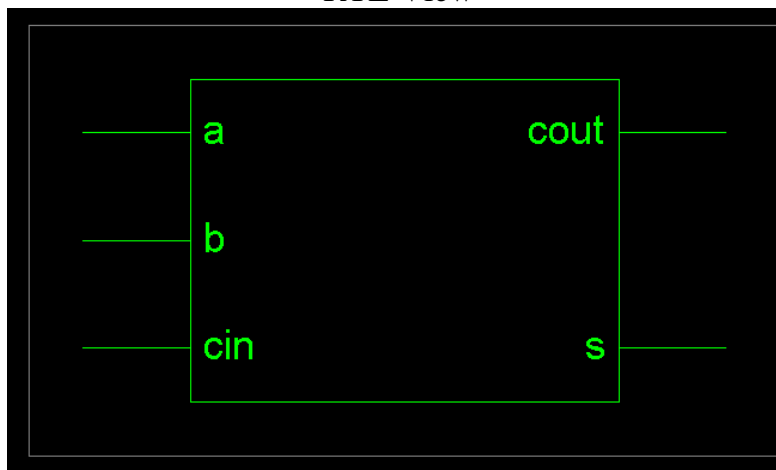

Simulation Waveform

 

## Quiz Questions with answer.

**Q.1** Who is the father of **VHDL**?

Ans. John Hines, Wright Patterson AFB, Dayton Ohio.

**Q.2** What is a test bench in **vhdl**?

Ans. A Test Bench in VHDL is code written in VHDL that provides stimulus for individual modules (also written in VHDL). Individual modules are instantiated by a single line of code showing the port.

**Q.3** How many inputs and output are used in Full adder?

Ans. Three inputs and two output.

**Q.4** What are the advantages of designing?

Ans. Advantages of Designing:

1. Designing is useful in quick implementation, testing and useful in complex circuits.
2. Designing reduces the design cycle.

**Q.5** Why HDL is used?

Ans. HDL is used because it is easy to design, implement, test and document increasingly complex digital system.

**Q.6** How many types of architecture in VHDL?

Ans: 4

## DIGITAL SYSTEM DESIGN (EE-326-F)

---

Q7. What is the difference between sequential and combinational ckts.?

Ans: Seq ckts have memory cell inside it and combinational has no memory in it.

Q8. Is it possible to construct full adder using half adder?

Ans: Yes, by using two half adders.

Q9. How many i/ps required for half subtractor?

Ans: Two, difference and a borrow.

Q10. Is it possible to construct full subtractor using half subtractor?

Ans: Yes, by using two half subtractor.

**EXPERIMENT No. 3(A)**


**Aim:- To Design a Multiplexer using VHDL**

**Multiplexer**

In digital circuit design, the selector wires are of digital value. In the case of a 2-to-1 multiplexer, a logic value of 0 would connect  $I_0$  to the output while a logic value of 1 would connect  $I_1$  to the output. In larger multiplexers, the number of selector pins is equal to  $\lceil \log_2(n) \rceil$  where  $n$  is the number of inputs.

A 4-to-1 multiplexer has a boolean equation where A, B, C and D are the two inputs,  $S_1$  and  $S_0$  are the select lines, and Y is the output:

S1	S0	Y
0	0	A
0	1	B
1	0	C
1	1	D

 

## Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

---- Uncomment the following library declaration if instantiating
---- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity abcd is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : in STD_LOGIC;
        d : in STD_LOGIC;
        s0 : in STD_LOGIC;
        s1 : in STD_LOGIC;
        y : out STD_LOGIC);
end abcd;


architecture Behavioral of abcd is

begin
  y <= a when s0 = '0' and s1 = '0' else
  b when s0 = '0' and s1 = '1' else
  c when s0 = '1' and s1 = '0' else
  d;


end Behavioral;
```

## OUTPUT:

RTL View

 

Simulation Waveform

 




## EXPERIMENT No. 3 (B)

**Aim:- To Design a Demultiplexer using VHDL**

### **Demultiplexer**

Demultiplexers take one data input and a number of selection inputs, and they have several outputs. They forward the data input to one of the outputs depending on the values of the selection inputs. Demultiplexers are sometimes convenient for designing general purpose logic, because if the demultiplexer's input is always true, the demultiplexer acts as a decoder.

I	S1	S0	ABCD
0	X	X	0000
1	0	0	1000
1	0	1	0100
1	1	0	0010
1	1	1	0001

 

## Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity dm is
  Port ( i : in  STD_LOGIC;
        s0 : in  STD_LOGIC;
        s1 : in  STD_LOGIC;
        a : out STD_LOGIC;
        b : out STD_LOGIC;
        c : out STD_LOGIC;
        d : out STD_LOGIC);
end dm;
```


```
architecture Behavioral of dm is
  signal p,q : STD_LOGIC;
begin
  p <= not s0;
  q <= not s1;

  a<= i and p and q;
  b<= i and q and s0;
  c<= i and p and s1;
  d<= i and s1 and s0;


end Behavioral;
```

## OUTPUT:

RTL View

 

## Simulation Waveform

 

## Quiz Questions with answer.

- Q.1 Name combinational logic circuit which sends data coming from a single source to two or more separate destinations.  
 Ans: Demultiplexer
- Q.2 What is the another name of Multiplexer.  
 Ans. Data Selector.
- Q.3 How many control lines will be used for a 8 – to – 1 multiplexer?  
 Ans. The number of control lines for an 8 to 1 Multiplexer is 3.
- Q.4 Which device changes serial data to parallel data .  
 Ans. The device which changes from serial data to parallel data is demultiplexer.
- Q.5 How many select lines will a 16 to 1 multiplexer will have?  
 Ans. 4
- Q6. Is it possible to construct 4:1 mux using two 2:1 mux?  
 Ans. Yes
- Q7. How many outputs are there in 1:8 mux?  
 Ans 8.
- Q8: What is the difference between sequential and combinational ckts.?  
 Ans: Seq ckts have memory cell inside it and combinational has no memory in it.
- Q9: What is the function of select line in mux?  
 Ans It selects the particular input to go on output.
- A10: What is the function of enable pin?  
 Ans: It enables the IC.


## EXPERIMENT No. 4

**Aim:- To Design an Encoder using VHDL**

**Encoder :**

An **encoder** is a device, circuit, transducer, software program, algorithm or person that converts information from one format or code to another, for the purposes of standardization, speed, secrecy, security, or saving space by shrinking size.

A3	A2	A1	A0	F1	F0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 


## Program:


```
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
entity encod1 is  
    Port ( a : in  STD_LOGIC_VECTOR (3 downto 0);  
          q : out STD_LOGIC_VECTOR (1 downto 0));  
end encod1;  
  
architecture Behavioral of encod1 is  
  
begin  
    q<="00" when a="0001" else  
      "01" when a="0010" else  
      "10" when a="0100" else  
      "11";  
  
end Behavioral;
```

## OUTPUT:

RTL View

 

## Simulation Waveform of Encoder

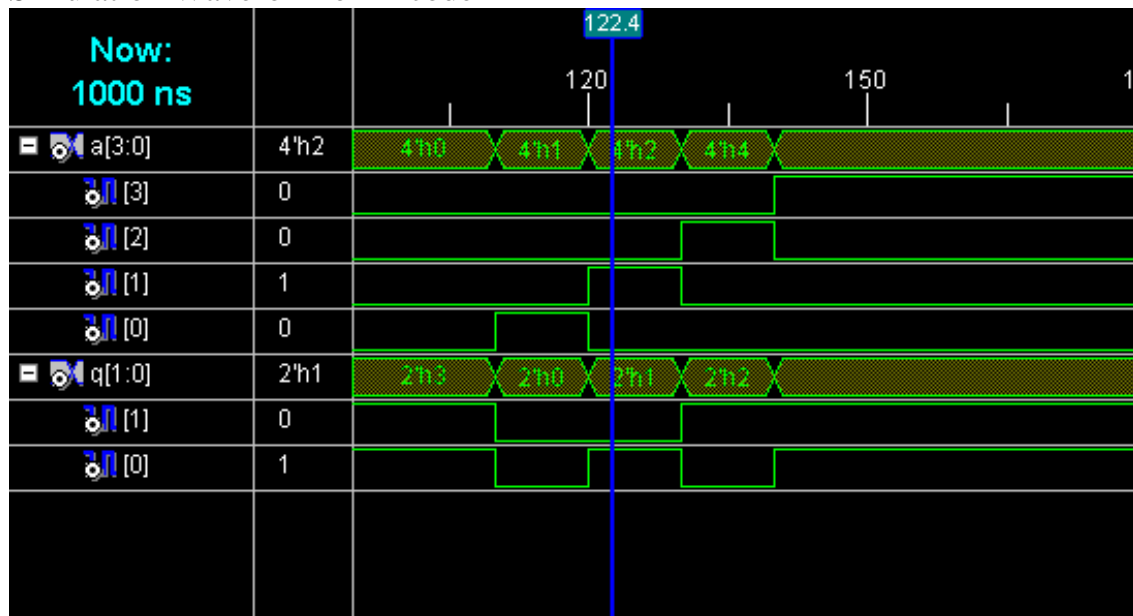

## Quiz Questions with answer.

- Q.1 Name the examples of combinational logic circuits.  
 Ans. Examples of common combinational logic circuits include: half adders, full adders, multiplexers, demultiplexers, encoders and decoders.
- Q.2 What do you mean by Digital Encoder?  
 Ans. Digital Encoder is a combinational circuit that generates a specific code at its outputs such as binary or BCD in response to one or more active inputs.
- Q.3 How many encoder are there in Digital Electronics?  
 Ans. There are two main types of digital encoder. The Binary Encoder and the Priority Encoder.
- Q.4 What is Combinational Logic?  
 Ans. Combinational Logic: A logic circuit in which the outputs are a function of the inputs. At any time, if you know the inputs, you can determine the outputs.
- Q.5 What is stable state?  
 Ans. Stable State: An internal or external signal maintains a constant magnitude (or specified range or function) for a period of time determined by external input signals.
- Q6. Write the applications of Encoder and decoder.  
 Ans: They are used in communication systems.
- Q7: Name some encoders.  
 Ans Priority encoder , 4:2 encoder and etc.
- Q8: How many i/ps are in 4:2 encoder?  
 Ans 4 i/ps and 2 o/ps.
- Q9: How many select lines are present in 2:4 decoder?  
 Ans none.

## EXPERIMENT No. 5

**Aim:- To Design a 2 to 4 Line Decoder using VHDL**


**Decoder:**

A **decoder** is a device which does the reverse of an encoder, undoing the encoding so that the original information can be retrieved. The same method used to encode is usually just reversed in order to decode.

In digital electronics, a decoder can take the form of a multiple-input, multiple-output logic circuit that converts coded inputs into coded outputs, where the input and output codes are different. Decoding is necessary in applications such as

EN	S1	S0	Z0	Z1	Z2	Z3
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 data multiplexing, 7 segment display and memory address decoding.



## Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

--library UNISIM;
--use UNISIM.VComponents.all;

entity decoder is
  Port ( en : in STD_LOGIC;
        s : in STD_LOGIC_VECTOR (1 downto 0);
        z : out STD_LOGIC_VECTOR (3 downto 0));
end decoder;


architecture arch of decoder is
  signal p,q : STD_Logic;
begin
  p <= not s(1);
  q <= not s(0);

  z(0) <= p and q;
  z(1) <= p and s(0);
  z(2) <= q and s(1);
  z(3) <= s(0) and s(1);

end arch;
```


## OUTPUT:

RTL View

 



## Simulation Waveform

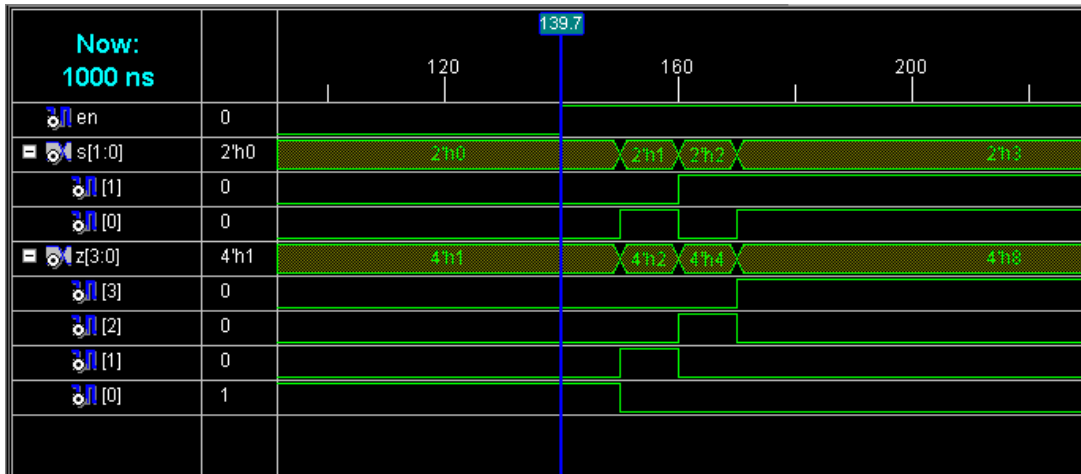

## Quiz Questions with answer.

Q.1 Name the examples of combinational logic circuits.

Ans. Examples of common combinational logic circuits include: half adders, full adders, multiplexers, demultiplexers, encoders and decoders.

Q.2 How many two-input AND and OR gates are required to realize  $Y=CD+EF+G$  ?

Ans  $Y=CD+EF+G$

Number of two input AND gates=2

Number of two input OR gates = 2

One OR gate to OR CD and EF and next to OR of G & output of first OR gate.

Q.3 Which device converts BCD to Seven Segment ?

Ans. A device which converts BCD to Seven Segment is called DECODER.

Q.4 What is a testbench in **vhdl**?

Ans. A Test Bench in VHDL is code written in VHDL that provides stimulus for individual modules (also written in VHDL). Individual modules are instantiated by a single line of code showing the port.

Q.5 What are the advantages of designing?

Ans. Advantages of Designing:

1. Designing is useful in quick implementation, testing and useful in complex circuits.
2. Designing reduces the design cycle.

Q6: Write the applications of Encoder and decoder.

Ans: They are used in communication systems.

Q7: Name some encoders.

Ans Priority encoder , 4:2 encoder and etc.

Q8: How many i/ps are in 4:2 encoder?

Ans 4 i/ps and 2 o/ps.

Q9: How many select lines are present in 2:4 decoder?

Ans none.


## EXPERIMENT No. 6

**Aim:- To Design a Down Counter using VHDL.**

 **Down Counter:**

In a binary up counter, a particular bit, except for the first bit, toggles if all the lower-order bits are 1's. The opposite is true for binary down counters. That is, a particular bit toggles if all the lower-order bits are 0's and the first bit toggles on every pulse.

Taking an example,  $A_4 A_3 A_2 A_1 = 0100$ . On the next count,  $A_4 A_3 A_2 A_1 = 0011$ .  $A_1$ , the lowest-order bit, is always complemented.  $A_2$  is complemented because all the lower-order positions ( $A_1$  only in this case) are 0's.  $A_3$  is also complemented because all the lower-order positions,  $A_2$  and  $A_1$  are 0's. But  $A_4$  is not complemented the lower-order positions,  $A_3 A_2 A_1 = 011$ , do not give an all 0 condition.



### Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

---- Uncomment the following library declaration if instantiating
---- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity up_counter is
    Port ( clk : in STD_LOGIC;
          sload : in STD_LOGIC;
          q : out STD_LOGIC_VECTOR (3 downto 0));
end up_counter;


architecture Behavioral of up_counter is
    signal tmp : std_logic_vector(3 downto 0);
begin
    process(clk)
    begin
        if(clk' event and clk = '1') then
            if sload = '0' then
                tmp <= "1111";
            else tmp <= tmp -1;

            end if;
        end if;
    end process;
    q <= tmp;


end Behavioral;
```

### OUTPUT:

RTL View

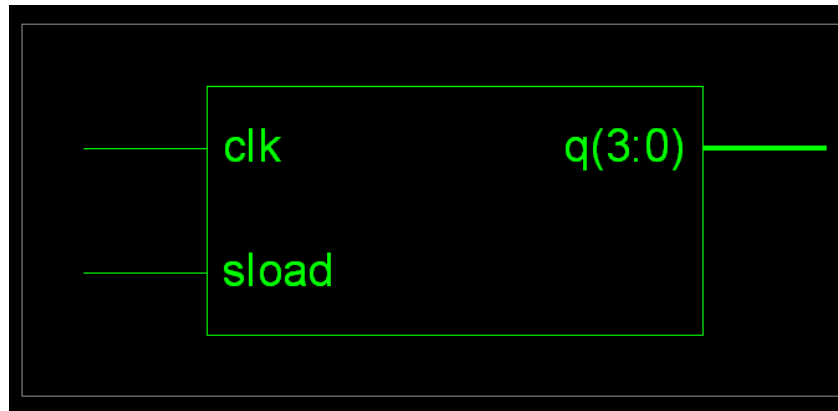

Simulation Waveform

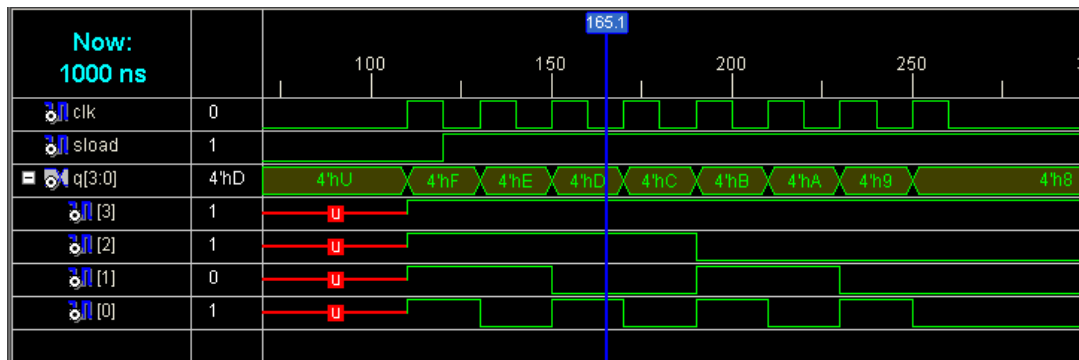

## Quiz Questions with answer.

- Q.1 What is sequential logic?  
 Ans. Sequential Logic: A logic circuit in which the outputs are a function of the present, and past inputs. The memory of past inputs involves the "state" of the system. At any time, if you know the present inputs, and state of the circuit, you can determine the outputs.
- Q.2 How many Flip-Flops are required for mod-16 counter?  
 Ans. The number of flip-flops is required for Mod-16 Counter is 4.
- Q.3 A 4-bit synchronous counter uses flip-flops with propagation delay times of 15 ns each. How much maximum possible time required for change of state?  
 Ans. 15 ns because in synchronous counter all the flip-flops change state at the same time.
- Q.4 How many flip flops are required to construct a decade counter?  
 Ans. Decade counter counts 10 states from 0 to 9 ( i.e. from 0000 to 1001 ). Thus four Flip Flop's are required.
- Q.5 How many flip-flops are required to construct mod 30 counter?  
 Ans. 5
- Q6: What is a flip flop?  
 Ans. It is memory element which stores previous data.
- Q7: What is the function of clock in counter ckt?  
 Ans: It synchronize the operation of flip flops in counter ckt.
- Q8: What is the maximum count for decade counter?

## DIGITAL SYSTEM DESIGN (EE-326-F)

---

Ans. From 0 to 9.

Q9: What is down counter?

Ans. When the qbar signal of previous ff is connected to clock of next ff.

Q10. What is the count for decade down counter?

Ans. From 9 to 0.

## EXPERIMENT No. 7

**Aim:- To Design a BCD to GRAY converter using VHDL**

**BCD to GRAY Converter:**


It is a digital circuit that converts BCD numbers into Gray codes.

2-bit Gray code
00
01
11
10
3-bit Gray code
000
001
011
010
110
111
101
100
4-bit Gray code
0000
0001
0011
0010
0110
0111
0101
0100
1100
1101
1111
1110
1010
1011
1001
1000


### Program:

```
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
---- Uncomment the following library declaration if instantiating  
---- any Xilinx primitives in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
entity bg is  
    Port ( i : in  STD_LOGIC_VECTOR (2 downto 0);  
          g : out STD_LOGIC_VECTOR (2 downto 0));  
end bg;  
  
architecture Behavioral of bg is  
  
begin  
process(i)  
begin  
case i is  
  
when "000" => g <= "000";  
when "001" => g <= "001";  
when "010" => g <= "011";  
when "011" => g <= "010";  
when "100" => g <= "110";  
when "101" => g <= "111";  
when "110" => g <= "101";  
when others => g <= "100";  
  
end case;  
  
end process;  
  
end Behavioral;
```

## OUTPUT:RTL View

 

## Simulation Waveform

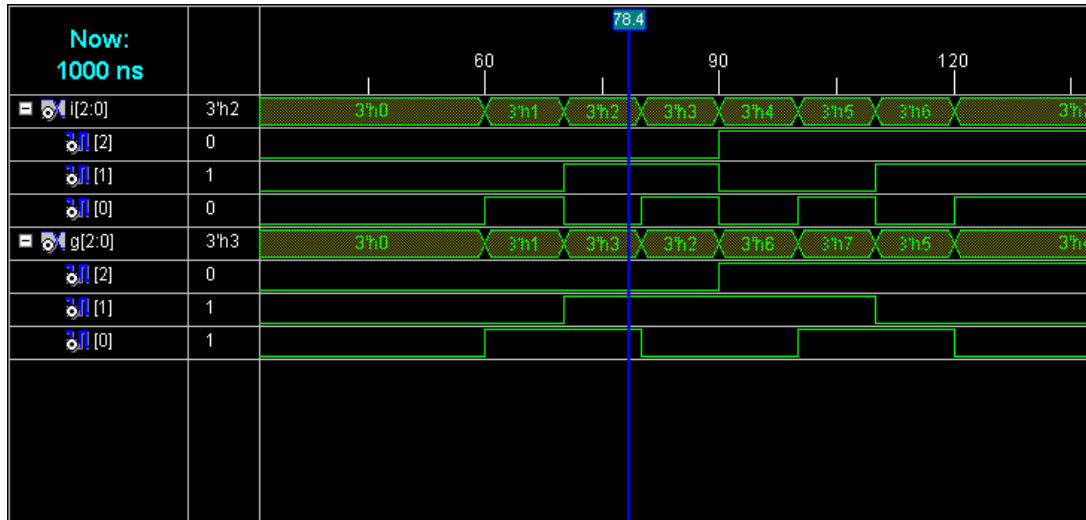

## Quiz Questions with answer.

- Q.1 What is VHDL?  
 Ans. VHDL is the VHSIC Hardware Description Language. VHSIC is an abbreviation for Very High Speed Integrated Circuit.
- Q.2 How many truth table entries are necessary for a four-input circuit?  
 Ans. 16
- Q.3 How many bits are there in BCD code?  
 Ans. 4
- Q.4 What is Combinational Logic?  
 Ans. Combinational Logic: A logic circuit in which the outputs are a function of the inputs. At any time, if you know the inputs, you can determine the outputs.
- Q.5 What is stable state?  
 Ans. Stable State: An internal or external signal maintains a constant magnitude (or specified range or function) for a period of time determined by external input signals.
- Q6. What is BCD to Gray converter?  
 Ans: The converter which converts bcd code into gray code.
- Q7: What is the application of above code converter?  
 Ans We use in communication systems.
- Q8. BCD to Gray converter is a combinational or sequential ckt?  
 Ans. Combinational ckt.



## DIGITAL SYSTEM DESIGN (EE-326-F)

---

Q9: Write down the method of Binary to Gray conversion.

Ans: Using the Ex-Or gates

Q10: Convert 0101 to Decimal.

Ans; 5

## EXPERIMENT No. 8

**Aim:- To Design a Toggle Flip Flop using VHDL.**

**T(Toggle) Flip Flop:**

If the T input is high, the T flip-flop changes state ("toggles") whenever the clock input is strobed. If the T input is low, the flip-flop holds the previous value. This behavior is described by the characteristic equation:

$$Q_{next} = T \oplus Q = T\bar{Q} + \bar{T}Q$$


T Flip-Flop operation							
<u>Characteristic table</u>				<u>Excitation table</u>			
<i>T</i>	<i>Q</i>	<i>Q<sub>next</sub></i>	Comment	<i>Q</i>	<i>Q<sub>next</sub></i>	<i>T</i>	Comment
0	0	0	hold state (no clk)	0	0	0	No change
0	1	1	hold state (no clk)	1	1	0	No change
1	0	1	Toggle	0	1	1	Complement
1	1	0	Toggle	1	0	1	Complement

### Program:

```
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
---- Uncomment the following library declaration if instantiating  
---- any Xilinx primitives in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
entity t_ff is  
    Port ( pr : in STD_LOGIC;  
          clr : in STD_LOGIC;  
          clk : in STD_LOGIC;  
          t : in STD_LOGIC;  
          q : inout STD_LOGIC;  
          qbar : out STD_LOGIC);  
end t_ff;  
  
architecture Behavioral of t_ff is  
begin  
    process(clk,clr,pr)  
    begin  
        if( pr='0' and clr ='1') then  
            q <= '1';  
        elsif ( pr ='1' and clr ='0') then  
            q <='0';  
        elsif(pr = '1' and clr ='1' and clk = '0' and clk' event)then  
            q <= (not t and q) or (not q and t);  
        end if;  
    end process;  
    qbar <= not q;  
  
end Behavioral;
```

### OUTPUT:

RTL View

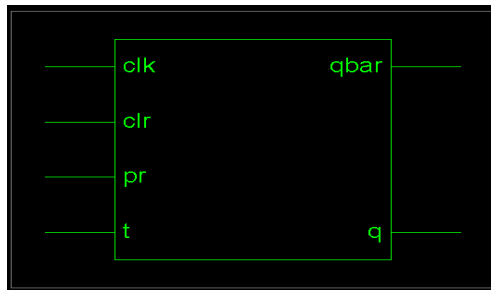

Simulation Waveform



## Quiz Questions with answer.

Q.1 Define flip-flop.

Ans. A flip-flop is a device that can maintain binary information until it is directed by an input signal to change its state. There are several different types of flip-flops, the more commonly used are the D-FF and the JK-FF. Flip-flops are used in sequential circuit design.

Q. 2The MSI chip 7474 is

Ans. MSI chip 7474 dual edge triggered D Flip-Flop.

Q. 3 How many flip-flops are required to construct mod 30 counter?

Ans 5

Q.4The output of SR flip flop when S=1, R=0 is

Ans As for the SR flip-flop S=set input R=reset input ,when S=1, R=0, Flip-flop will be set.

Q.5 The number of flip flops contained in IC 7490 is

Ans 2.

Q6 What are the I/Ps of JK flip-flop where this race round condition occurs?

Ans; .Both the inputs are 1

Q7: .Flip flop is astable or bistable?

Ans Bistable.

Q8: When RS flip-flop is said to be in a SET state?

Ans. When the output is 1

Q9: What is the function of clock signal in flip-flop?

Ans. To get the output at known time.

Q10: What is the advantage of JK flip-flop over RS flip-flop?

Ans. In RS flip-flop when both the inputs are 1 output is undetermined.

## EXPERIMENT No. 9

**Aim:-Implement Half Adder using FPGA & CPLD.**

**Program:**

```
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
---- Uncomment the following library declaration if instantiating  
---- any Xilinx primitives in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
entity ha is  
  Port ( a : in STD_LOGIC;  
        b : in STD_LOGIC;  
        s : out STD_LOGIC;  
        c : out STD_LOGIC);  
end ha;  
  
architecture Behavioral of ha is  
begin  
s <= a xor b;  
c <= a and b;  
end Behavioral;
```

## Output

Inputs		Outputs	
<i>A</i>	<i>B</i>	<i>C</i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

## DIGITAL SYSTEM DESIGN (EE-326-F)

---

### **Quiz Questions with answer.**

Q.1 Who is the father of VHDL?

Ans. John Hines, Wright Patterson AFB, Dayton Ohio.

Q.2 What is a testbench in vhdl?

Ans. A Test Bench in VHDL is code written in VHDL that provides stimulus for individual modules (also written in VHDL). Individual modules are instantiated by a single line of code showing the port.

Q.3 How many inputs and output are used in Full adder?

Ans. Three inputs and two output.

Q.4 What are the advantages of designing?

Ans. Advantages of Designing:

1. Designing is useful in quick implementation, testing and useful in complex circuits.

2. Designing reduces the design cycle.

Q.5 Why HDL is used?

Ans. HDL is used because it is easy to design, implement, test and document increasingly complex digital system.

Q.6 Give the basic rules for binary addition?

Ans.  $0+0 = 0$ ;  $0+1 = 1$ ;  $1+1 = 10$ ;  $1+0 = 1$ .

Q.7: What is the drawback of half adder?

Ans: We can't add carry bit from previous stage.

Q.8: What is the difference b/w half adder & half subtractor?

Ans: Half adder can add two bits & half subtractor can subtract two bits.

Q.9: Define Nibble?

Ans. Combination of four bits

## EXPERIMENT No. 10

**Aim:-Implement Full Adder using FPGA & CPLD.**

### Full adder


A **full adder** is a logical circuit that performs an addition operation on three one-bit binary numbers often written as  $A$ ,  $B$ , and  $C_{in}$ . The full adder produces a two-bit output sum typically represented with the signals  $C_{out}$  and  $S$  where

$$sum = 2 \times C_{out} + S.$$

The full adder's truth table is:

Truth Table:

Inputs			Outputs	
$A$	$B$	$C_i$	$C_o$	$S$
0	0	0	0	0
1	0	0	0	1
0	1	0	0	1
1	1	0	1	0
0	0	1	0	1
1	0	1	1	0
0	1	1	1	0
1	1	1	1	1

 



## DIGITAL SYSTEM DESIGN (EE-326-F)

---

### Program:

```
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
---- Uncomment the following library declaration if instantiating  
---- any Xilinx primitives in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
entity fa is  
  Port ( a : in STD_LOGIC;  
        b : in STD_LOGIC;  
        cin : in STD_LOGIC;  
        s : out STD_LOGIC;  
        cout : out STD_LOGIC);  
end fa;  
  
architecture Behavioral of fa is  
  
begin  
s <= (a xor b) xor cin;  
cout <= (a and b) or (b and cin) or (a and cin);  
  
end Behavioral;
```

### OUTPUT:

Inputs			Outputs	
<i>A</i>	<i>B</i>	<i>C<sub>i</sub></i>	<i>C<sub>o</sub></i>	<i>S</i>
0	0	0	0	0
1	0	0	0	1
0	1	0	0	1
1	1	0	1	0
0	0	1	0	1
1	0	1	1	0
0	1	1	1	0
1	1	1	1	1

### Quiz Questions with answer.

Q.1 Who is the father of VHDL?

Ans. John Hines, Wright Patterson AFB, Dayton Ohio.

Q.2 What is a testbench in vhdL?

Ans. A Test Bench in VHDL is code written in VHDL that provides stimulus for individual modules (also written in VHDL). Individual modules are instantiated by a single line of code showing the port.

Q.3 How many inputs and output are used in Full adder?

Ans. Three inputs and two output.

Q.4 What are the advantages of designing?

Ans. Advantages of Designing:

1. Designing is useful in quick implementation, testing and useful in complex circuits.

2. Designing reduces the design cycle.

Q.5 Why HDL is used?

Ans. HDL is used because it is easy to design, implement, test and document increasingly complex digital system.

Q.6 Give the basic rules for binary addition?

Ans.  $0+0 = 0$ ;  $0+1 = 1$  ;  $1+1 = 1 0$  ;  $1+0 = 1$ .

Q.7: What is the drawback of half adder?

Ans: We can't add carry bit from previous stage.

Q.8: What is the difference b/w half adder& half sub tractor?

Ans: Half adder can add two bits & half sub tractor can subtract two bits.

Q.9: Define Nibble?

Ans. Combination of four bits

## EXPERIMENT No. 11

**Aim:- Implement Delay Flip-Flop using FPGA & CPLD.**

### **Flip-Flops:**

In digital circuits, a **flip-flop** is a term referring to an electronic circuit (a bistable multivibrator) that has two stable states and thereby is capable of serving as one bit of memory. Today, the term *flip-flop* has come to mostly denote *non-transparent* (*clocked* or *edge-triggered*) devices

A flip-flop is usually controlled by one or two control signals and/or a gate or clock signal. The output often includes the complement as well as the normal output.

### **D(Delay) Flip-Flop:**

The D flip-flop is the most common flip-flop in use today. It is better known as *delay* flip-flop

The Q output always takes on the state of the D input at the moment of a positive edge (or negative edge if the clock input is active low).<sup>[7]</sup> It is called the **D** flip-flop for this reason, since the output takes the value of the **D**input or *Data* input, and *Delays* it by maximum one clock count. The D flip-flop can be interpreted as a primitive memory cell, [zero-order hold](#), or [delay line](#). Whenever the clock pulses, the value of  $Q_{next}$  is D and  $Q_{prev}$  otherwise.

Truth table:

<b>Clock</b>	<b>D</b>	<b>Q</b>	<b>Q<sub>prev</sub></b>
Rising edge	0	0	X
Rising edge	1	1	X
Non-Rising	X	Q <sub>prev</sub>	

### Program:

```
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
---- Uncomment the following library declaration if instantiating  
---- any Xilinx primitives in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
entity d_ff is  
    Port ( clk : in STD_LOGIC;  
          clr : in STD_LOGIC;  
          d : in STD_LOGIC;  
          pr : in STD_LOGIC;  
          q : out STD_LOGIC);  
end d_ff;  
  
architecture Behavioral of d_ff is  
begin  
    process(clk,clr,pr)  
    begin  
        if( pr='0' and clr ='1') then  
            q<= '1';  
        elsif ( pr ='1' and clr ='0') then  
            q<='0';  
        elsif(pr = '1' and clr ='1'and falling_edge(clk))then  
            q<= d;  
        end if;  
    end process;  
  
end Behavioral;
```

**OUTPUT:**

<b>Clock</b>	<b>D</b>	<b>Q</b>	<b>Q<sub>prev</sub></b>
Rising edge	0	0	X
Rising edge	1	1	X
Non-Rising	X	Q <sub>prev</sub>	

**Quiz Questions with answer.**

Q.1 Define flip-flop.

Ans. A flip-flop is a device that can maintain binary information until it is directed by an input signal to change its state. There are several different types of flip-flops, the more commonly used are the D-FF and the JK-FF. Flip-flops are used in sequential circuit design.

Q. 2The MSI chip 7474 is

Ans. MSI chip 7474 dual edge triggered D Flip-Flop.

Q. 3 How many flip-flops are required to construct mod 30 counter?

Ans 5

Q.4The output of SR flip flop when S=1, R=0 is

Ans As for the SR flip-flop S=set input R=reset input ,when S=1, R=0, Flip-flop will be set.

Q.5 The number of flip flops contained in IC 7490 is

Ans 2.

Q6 What are the I/Ps of JK flip-flop where this race round condition occurs?

Ans; .Both the inputs are 1

Q7: .Flip flop is astable or bistable?

Ans Bistable.

Q8: When RS flip-flop is said to be in a SET state?

Ans. When the output is 1

Q9: What is the function of clock signal in flip-flop?

Ans. To get the output at known time.

Q10: What is the advantage of JK flip-flop over RS flip-flop?


Ans. In RS flip-flop when both the inputs are 1 output is undetermined.

## EXPERIMENT No. 12

**Aim:- Implement BCD to 7 segment Decoder using FPGA & CPLD.**
 
### **BCD to 7 segment Decoder:**

It is a digital circuit that decodes BCD numbers into 7 segment numbers that can be used for 7 segment displays and other applications.



INPUTS	OUTPUT						
	A	B	C	d	e	f	G
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	1	0	1	1

### Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

---- Uncomment the following library declaration if instantiating
---- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity bs is
    Port ( i : in  STD_LOGIC_VECTOR (3 downto 0);
          o : out STD_LOGIC_VECTOR (6 downto 0));
end bs;

architecture Behavioral of bs is

begin

o <= "1111110" when i ="0000" else
    "0110000" when i ="0001" else
    "1101101" when i ="0010" else
    "1111001" when i ="0011" else
    "0110011" when i ="0100" else
    "1011011" when i ="0101" else
    "1011111" when i ="0110" else
    "1110000" when i ="0111" else
    "1111111" when i ="1000" else
    "1111011" when i ="1001";
end Behavioral;

OUTPUT:
```

## DIGITAL SYSTEM DESIGN (EE-326-F)

---

INPUTS	OUTPUT						
	A	B	C	d	e	f	G
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	1	0	1	1

### QUIZ QUESTIONS WITH ANSWERS.

Q.1 Name the examples of combinational logic circuits.

Ans. Examples of common combinational logic circuits include: half adders, full adders, multiplexers, demultiplexers, encoders and decoders.  
One OR gate to OR CD and EF and next to OR of G & output of first OR gate.

Q.2 Which device converts BCD to Seven Segment ?

Ans. A device which converts BCD to Seven Segment is called DECODER.

Q.3 What is BCD to Seven segment decoder?

Ans. A binary coded decimal (BCD) to 7-segment display decoder such as the TTL 74LS47 or 74LS48, have 4 BCD inputs and 7 output lines, one for each LED segment. This allows a smaller 4-bit binary number (half a byte) to be used to display all the ternary numbers from 0 to 9 and by adding two displays together; a full range of numbers from 00 to 99 can be displayed with just a single byte of 8 data bits.

Q.4 What is decoder?

Ans. A Decoder IC, is a device which converts one digital format into another and the most commonly used device for doing this is the Binary Coded Decimal (BCD) to 7-Segment Display Decoder.

Q5: Q.5 What are the advantages of designing?

Ans. Advantages of Designing:

1. Designing is useful in quick implementation, testing and useful in complex circuits.
2. Designing reduces the design cycle.

Q6: Write the applications of Encoder and decoder.

Ans: They are used in communication systems.

Q7: Name some encoders.

Ans Priority encoder , 4:2 encoder and etc.

Q8: How many i/ps are in 4:2 encoder?

Ans 4 i/ps and 2 o/ps.

Q9: How many select lines are present in 2:4 decoder?

Ans none.

Q10: How many outputs are present in 3:8 decoder?

Ans. 8.



## EXPERIMENT No. 13


**Aim:- Implement an Up Counter using FPGA & CPLD.**

### **Up Counter:**

A synchronous binary counter counts from 0 to  $2^N-1$ , where N is the number of bits/flip-flops in the counter. Each flip-flop is used to represent one bit. The flip-flop in the lowest-order position is complemented/toggled with every clock pulse and a flip-flop in any other position is complemented on the next clock pulse provided all the bits in the lower-order positions are equal to 1.

Take for example  $A_4 A_3 A_2 A_1 = 0011$ . On the next count,  $A_4 A_3 A_2 A_1 = 0100$ .  $A_1$ , the lowest-order bit, is always complemented.  $A_2$  is complemented because all the lower-order positions ( $A_1$  only in this case) are 1's.  $A_3$  is also complemented because all the lower-order positions,  $A_2$  and  $A_1$  are 1's. But  $A_4$  is not complemented the lower-order positions,  $A_3 A_2 A_1 = 011$ , do not give an all 1 condition.

 To implment a synchronous counter, we need a flip-flop for every bit and an AND gate for every bit except the first and the last bit. The diagram below shows the implementation of a 4-bit synchronous up-counter.



## DIGITAL SYSTEM DESIGN (EE-326-F)

---

### **Program:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

--library UNISIM;
--use UNISIM.VComponents.all;

entity up_counter is
  Port ( clk : in STD_LOGIC;
        sload : in STD_LOGIC;
        clr : in STD_LOGIC;
        q : out STD_LOGIC_VECTOR (3 downto 0));
end up_counter;

architecture Behavioral of up_counter is
  signal tmp : std_logic_vector(3 downto 0);
begin
  process(clk)
  begin
    if(clk' event and clk = '1') then
      if clr = '0' then
        tmp <= "0000";
      elsif sload = '1' then
        if tmp = "1010" then
          tmp <= "0000";
        else tmp <= tmp +1;

        end if;
      end if;
    end if;
  end process;
  q <= tmp;
end Behavioral;
```

### QUIZ QUESTIONS WITH ANSWERS.

Q.1 What is sequential logic?

Ans. Sequential Logic: A logic circuit in which the outputs are a function of the present, and past inputs. The memory of past inputs involves the "state" of the system. At any time, if you know the present inputs, and state of the circuit, you can determine the outputs.

Q.2 How many Flip-Flops are required for mod-16 counter?

Ans. The number of flip-flops is required for Mod-16 Counter is 4.

Q.3 A 4-bit synchronous counter uses flip-flops with propagation delay times of 15 ns each. How much maximum possible time required for change of state?

Ans. 15 ns because in synchronous counter all the flip-flops change state at the same time.

Q.4 How many flip flops are required to construct a decade counter?

Ans. Decade counter counts 10 states from 0 to 9 ( i.e. from 0000 to 1001 ). Thus four Flip Flop's are required.

Q.5 How many flip-flops are required to construct mod 30 counter?

Ans 5

Q6: What is a flip flop?

Ans. It is memory element which stores previous data.

Q7: What is the function of clock in counter ckt?

Ans: It synchronize the operation of flip flops in counter ckt.

Q8: What is the maximum count for decade counter?

Ans. From 0 to 9.

Q9: What is down counter?

Ans. When the qbar signal of previous ff is connected to clock of next ff.

Q10. What is the count for decade down counter?


Ans. From 9 to 0.

## EXPERIMENT No. 14

**Aim:- Implement a 1-bit Comparator using FPGA & CPLD.**

 **Comparator :**

In electronics, a **comparator** is a device which compares two voltages or currents and switches its output to indicate which is larger.



A	B	AGB	AEB	ALB
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

### Program:

```
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
---- Uncomment the following library declaration if instantiating  
---- any Xilinx primitives in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
entity compare is  
    Port ( a : in STD_LOGIC;  
          b : in STD_LOGIC;  
          agb : out STD_LOGIC;  
          aeb : out STD_LOGIC;  
          alb : out STD_LOGIC);  
end compare;  
  
architecture Behavioral of compare is  
    signal p,q : std_logic;  
begin  
    p <= not a;  
    q <= not b;  
    agb <= a and q;  
    aeb <= (a and b) or (p and q);  
    alb <= p and b;  
end Behavioral;
```

### QUIZ QUESTIONS WITH ANSWERS.

Q.1 What is Identity Comparator?

Ans. Identity Comparator - an *Identity Comparator* is a digital comparator that has only one output terminal for when  $A = B$  either "HIGH"  $A = B = 1$  or "LOW"  $A = B = 0$

Q.2 What is Magnitude Comparator?

Ans. Magnitude Comparator - a *Magnitude Comparator* is a type of digital comparator that has three output terminals, one each for equality,  $A = B$  greater than,  $A > B$  and less than  $A < B$ .

Q.3: Q.3How many inputs and output are used in Full adder?

Ans. Three inputs and two output.

Q.4 What are the advantages of designing?

Ans. Advantages of Designing:

1. Designing is useful in quick implementation, testing and useful in complex circuits.
2. Designing reduces the design cycle.

Q.5 Why HDL is used?

## DIGITAL SYSTEM DESIGN (EE-326-F)

---

Ans. HDL is used because it is easy to design, implement, test and document increasingly complex digital system.

Q6. How many types of architecture in VHDL?

Ans: 4

Q7. What is the difference between sequential and combinational ckts.?

Ans: Seq ckts have memory cell inside it and combinational has no memory in it.

Q8. Is it possible to construct full adder using half adder?

Ans: Yes, by using two half adders.

Q9. How many i/ps required for half subtractor?

Ans: Two, difference and a borrow.

Q10. Is it possible to construct full subtractor using half subtractor?

Ans: Yes, by using two half subtractor.

## EXPERIMENT No. 15

**Aim:- Implement an ALU using FPGA & CPLD.**

**ALU :**

In computing, an **arithmetic logic unit (ALU)** is a digital circuit that performs arithmetic and logical operations. The ALU is a fundamental building block of the central processing unit (CPU) of a computer, and even the simplest microprocessors contain one for purposes such as maintaining timers. The processors found inside modern CPUs and graphics processing units (GPUs) accommodate very powerful and very complex ALUs; a single component may contain a number of ALUs.

The inputs to the ALU are the data to be operated on (called operands) and a code from the control unit indicating which operation to perform. Its output is the result of the computation.

**Program:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

---- Uncomment the following library declaration if instantiating
---- any Xilinx primitives in this code.
--library UNISIM;

entity alu_1 is
  Port ( a : in STD_LOGIC_VECTOR (3 downto 0);
        b : in STD_LOGIC_VECTOR (3 downto 0);
        op : in STD_LOGIC_VECTOR (2 downto 0);
        y : out STD_LOGIC_VECTOR (7 downto 0));
end alu_1;
architecture Behavioral of alu_1 is
begin
y<=("0000"&a) + ("0000"&b) when op="000" else
  ("0000"&a) - ("0000"&b) when op="001" else
  a*b when op="010" else
  ("0000"&a) and ("0000"&b) when op="011" else
  ("0000"&a) or ("0000"&b) when op="100" else
  ("0000"&a) xor ("0000"&b) when op="101" else
  ("0000"&a) nor ("0000"&b) when op="110" else
  ("0000"&a) nand ("0000"&b) when op="111";

end Behavioral;
```

## DIGITAL SYSTEM DESIGN (EE-326-F)

---

Q.1 What is VHDL?

Ans. VHDL is the VHSIC Hardware Description Language. VHSIC is an abbreviation for Very High Speed Integrated Circuit.

Q.2 How many truth table entries are necessary for a four-input circuit?

Ans. 16

Q.3 What input values will cause an AND logic gate to produce a HIGH output?

Ans. All inputs of AND gate must be HIGH.

Q.4 Name all the basic gates.

Ans. i) AND ii) OR iii) NOT

Q.5 Name all the universal gates.

Ans. i) NAND ii) NOR

Q.6 What is the full form of IEEE?

Ans. Institute of Electrical and Electronic Engineering.

Q.7 What is the full form of ASCII?

Ans. American Standard Code for information Interchange.

Q.8 Define Entity.

Ans. It is an external view of a design unit.

Q.9 Why NAND and NOR are called universal gates?

Ans. Because all the basic gates can be derive from them.

Q.10 How many architectures are present in VHDL.

Ans. 4, behavior, dataflow, structural and mixed.