

(220-EL-211761)

Roll No.

PAPER ID—10715

B.Tech. EXAMINATION, 2024

(Second Semester)

ELECTRICAL AND ELECTRONICS
ENGINEERING

Code : ECE-102

Electronics Engineering-I

Time : 3 Hours

Maximum Marks : 70

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

Note : Attempt *Five* questions in all. Q. No. **1** is compulsory. All questions carry equal marks.

1. (a) Define Wiedmann-Franz law.
- (b) What is Continuity Equation ?

- (c) Differentiate between clippers and clampers circuit.
- (d) Give the application of UJT.
- (e) What is Zener Diode ?
- (f) What is voltage divider bias ?
- (g) What are voltage multiplier circuits ?

7×2=14

2. A sinusoidal voltage of 230 V is applied to a half-wave rectifier circuit through a transformer of turn ratio 25 : 1. The load resistance value is 1 K Ω and diode internal resistance is 10 Ω . Determine (i) I_m , I_{dc} and I_{rms} (ii) Rectifier efficiency (iii) dc output power (iv) dc output voltage (v) ac input power (vi) Peak Inverse Voltage. **14**
3. Explain light emitting diodes, semiconductor lasers, and light emitting materials. **14**
4. Explain construction and working of Construction and working of DIAC and TRIAC **14**

5. Draw the input and output characteristics of CE and CB configuration in detail. **14**
6. Calculate operating point for the same characteristics with proper labeling of the diagram of each circuit. **14**
7. What is the difference between JFET and MOSFET ? Explain the working of Depletion type of MOSFET and its characteristics. **14**

PAPER ID—10715

B. Tech. (VLSI/ECE/EEE all Elect)

EXAMINATION, 2023

(Second Semester)

ELECTRONICS ENGINEERING-I

Time : 3 Hours

Maximum Marks : 70

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

Note : Attempt *Five* questions in all. Q. No. 1 is compulsory. All questions carry equal marks.

1. (a) What is mean free path and mobility ?
- (b) What are SI and Ge materials used in semiconductors ?
- (c) Differentiate between clippers and clampers circuit.

- (d) What is the difference between JFET and MOSFET ?
- (e) What is Zener diode ?
- (f) What is transistor power dissipation ?
- (g) What is small signal model of MOSFET ?

7×2=14

2. A sinusoidal voltage of 230 V is applied to a half-wave rectifier circuit through a transformer of turn ratio 25 : 1. The load resistance value is $1\text{ K}\Omega$ and diode internal resistance is 10Ω . Determine (i) I_m , I_{dc} and I_{rms} (iv) Rectifier efficiency (ii) dc output power (v) dc output voltage (iii) ac input power (vi) Peak Inverse Voltage. **14**
3. Explain Photodiodes, photo detectors and solar cell. **14**
4. Explain construction and working of construction and working of SCR (Semiconductor Controlled Rectifier). **14**

5. Explain in detail the CE configuration characteristics input characteristics and output characteristics with proper labelling of the diagram of each circuit. **14**
6. What is the difference between JFET and MOSFET ? Explain the working of Depletion type of MOSFET and its characteristics. **14**

PAPER ID—10715

B. Tech. (VLSI/ECE/EEE all Elect)

EXAMINATION, 2023

(Second Semester)

ELECTRONICS ENGINEERING-I

Time : 3 Hours

Maximum Marks : 70

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

Note : Attempt *Five* questions in all. Q. No. 1 is compulsory. All questions carry equal marks.

1. (a) What is mean free path and mobility ?
- (b) What are SI and Ge materials used in semiconductors ?
- (c) Differentiate between clippers and clampers circuit.

- (d) What is the difference between JFET and MOSFET ?
- (e) What is Zener diode ?
- (f) What is transistor power dissipation ?
- (g) What is small signal model of MOSFET ?

7×2=14

2. A sinusoidal voltage of 230 V is applied to a half-wave rectifier circuit through a transformer of turn ratio 25 : 1. The load resistance value is $1\text{ K}\Omega$ and diode internal resistance is 10Ω . Determine (i) I_m , I_{dc} and I_{rms} (iv) Rectifier efficiency (ii) dc output power (v) dc output voltage (iii) ac input power (vi) Peak Inverse Voltage. **14**
3. Explain Photodiodes, photo detectors and solar cell. **14**
4. Explain construction and working of construction and working of SCR (Semiconductor Controlled Rectifier). **14**

5. Explain in detail the CE configuration characteristics input characteristics and output characteristics with proper labelling of the diagram of each circuit. **14**
6. What is the difference between JFET and MOSFET ? Explain the working of Depletion type of MOSFET and its characteristics. **14**